

BOOLEAN ALGEBRA

Axioms and laws of Boolean Algebra

<u>Axioms</u>	<u>OR</u>	<u>Addition</u>	<u>Complement</u>
<u>Nullification</u>			
$0 \cdot 0 = 0$	$0 + 0 = 0$	$\bar{1} = 0$	
$0 \cdot 1 = 0$	$0 + 1 = 1$	$\bar{0} = 1$	
$1 \cdot 0 = 0$	$1 + 0 = 1$		
$1 \cdot 1 = 1$	$1 + 1 = 1$		

Laws of Boolean Algebra

AND laws

- $x \cdot 0 = 0$
- $x \cdot 1 = x$
- $x \cdot x = x$
- $x \cdot \bar{x} = 0$

OR LAWS

- $x + 0 = x$
- $x + 1 = 1$
- $x + x = x$
- $x + \bar{x} = 1$

COMPLEMENTATION LAW (Double Negation Law)

$\overline{\bar{x}} = x$

Commutative Law

$x + y = y + x$

$x \cdot y = y \cdot x$

Associative Law

$x + (y + z) = (x + y) + z$

$x \cdot (y \cdot z) = (x \cdot y) \cdot z$

Distributive Law

$x + (y \cdot z) = (x + y) \cdot (x + z)$

$x \cdot (y + z) = x \cdot y + x \cdot z$

$x \cdot x = x$

$x + x = x$

Negation Law

$x \cdot \bar{x} = 0$

$x + \bar{x} = 1$

Null Law

$x \cdot 0 = 0$

$x + 0 = x$

Absorption Law:

$$x + x \cdot y = x$$

$$x \cdot (x + y) = x$$


De Morgan's Theorem

$$\overline{x+y} = \bar{x} \cdot \bar{y}$$

$$x \cdot \bar{y} = \overline{\bar{x} + y}$$

Duality

changes

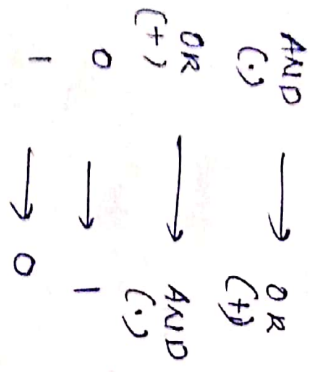

Ex:-

$$A \cdot 1 = A$$

$$A + 0 = A$$

$$\overline{x+y} = \bar{x} \cdot \bar{y}$$

$$x \cdot \bar{y} = \overline{\bar{x} + y}$$

$\Rightarrow$  Demorganize or Apply Demorgan's Theorem to find complement or the following expression.

$$\overline{(A+B)} = (\bar{A} \cdot \bar{B})$$

$$\overline{(A+B) \cdot (C+D)} = (\overline{A+B}) + (\overline{C+D})$$

$$= (\bar{A} \cdot \bar{B}) + (\bar{C} \cdot \bar{D})$$

$$= \bar{A} \cdot \bar{B} + \bar{C} \cdot \bar{D}$$

$$\left. \begin{aligned} \overline{x+y} &= \bar{x} \cdot \bar{y} \\ x \cdot \bar{y} &= \overline{\bar{x} + y} \\ \bar{x} &= x \end{aligned} \right\}$$

2.  $\overline{A \cdot B} + \bar{A} + A \cdot B = \bar{A} + B + A$

$$x \cdot \bar{y} = \overline{\bar{x} + y}$$

$$\overline{A \cdot B} + \bar{A} + A \cdot B = \bar{A} + A + \bar{A} + A \cdot B$$

2.  $\overline{A \cdot B} + \bar{A} + A \cdot B = \overline{A \cdot B} + \bar{A} + A \cdot B$

Demorgan's Law

$AB \cdot A$
$A \cdot B \cdot A$
$A \cdot A \cdot B$
$AB$

$$= \bar{A} \cdot \bar{A} + \bar{A} + A \cdot B$$

$$= AB \cdot A \cdot \bar{A} B$$

$$= AB \cdot \bar{A} B$$

$$= 0$$

3.  $\overline{A \cdot B} + \bar{B} + A = 0$

$$F = \overline{A \cdot B} + \bar{B} + A$$

$$= \overline{A \cdot B} + \bar{B} + A$$

$$= \overline{A \cdot B} + \bar{B} + A$$

[Demorgan's Law]

$$4. \quad x(y+z) = x(y+z)$$

$$= \frac{x(y+z)}{x(y+z)} = \bar{x} + (\overline{y+z})$$

$$= \bar{x} + (\overline{y \cdot z})$$

⇒ simplify the following Boolean expression  
or Boolean function using laws of Boolean Algebra.

$$1. \quad x(\bar{x}+y)$$

$$= x\bar{x} + x \cdot y \quad (\text{Distributive law})$$

$$= 0 + xy$$

$$= \underline{xy} \quad (x \cdot \bar{x} = 0)$$

$$2. \quad AB + A(B+C) + B(B+C)$$

$$= \overset{AB}{AB} + A \cdot B + A \cdot C + B \cdot B + B \cdot C$$

$$= AB + AB + A \cdot C + B + B \cdot C \quad \rightarrow (x \cdot x = x)$$

$$= AB + A \cdot (B+C) + B + B \cdot C$$

$$= AB + A(B+C) + B + B \cdot C$$

$$= AB + AB + AC + B$$

$$= AB + AC + B$$

$$= AC + \overbrace{BA}^{xy+x} + B$$

$$= AC + B$$

(Absorption law)

$$3. \quad (x+y)(x+y')$$

$$4. \quad xy + xy'$$

$$5. \quad ABC [AB + \bar{C}(B+C)]$$

⇒ Prove the following Boolean identity using laws of Boolean Algebra.

$$LHS = x + x'y$$

$$= (x + x') \cdot (x + y) \quad (x + (x' \cdot y))$$

$$= 1 \cdot (x + y) \quad (Distributive law)$$

$$= (x + y)$$

$$\therefore LHS = RHS$$



- $AB + \bar{A}C : (A+B)(\bar{A}+C)$
- $AB + \bar{A}C + A\bar{B}C (A+B+C) = 1$
- $\bar{A}\bar{B} + \bar{A} + AB$


Logic Gates

Universal gates

AND OR NOT  
NAND, NOR - we can do all basic operations AND OR NOT using universal gts

1. AND gate (All or nothing gate)

inp	o/p
A B	$y = A \cdot B$
0 0	0
0 1	0
1 0	0
1 1	1

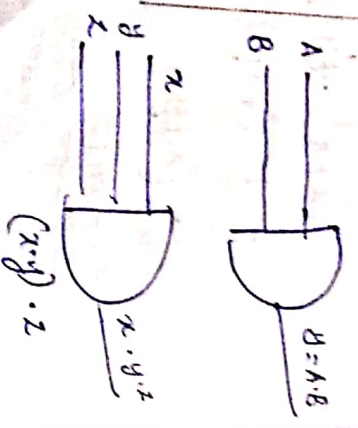

2. OR gate (Any or all gate)

A	B	$y = A + B$
0	0	0
0	1	1
1	0	1
1	1	1



3. NOT (Inverter)  $y = \bar{A}$

A	$y = \bar{A}$
0	1
1	0





Universal Gates

4. NAND gate

NAND  $\rightarrow$  NOT AND

A	B	$y = \overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0

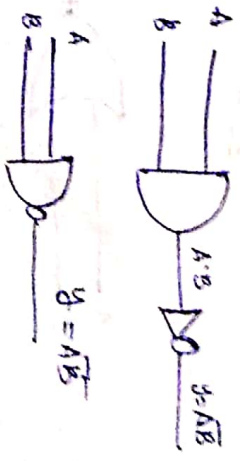

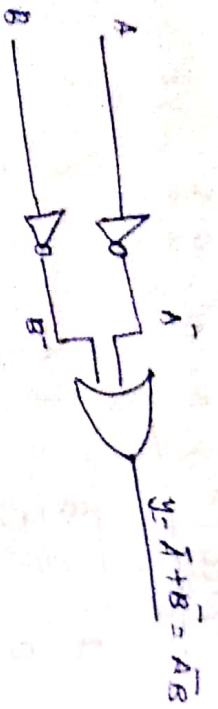

Negative  
or gate  
Bubble  
got

5. NOR gate

A	B	$y = A + \bar{B}$
0	0	1
0	1	0
1	0	0
1	1	0



Special gates

6. XOR Gate  $\Rightarrow y = A \oplus B$   
 $= \bar{A}B + A\bar{B}$

A	B	$y = A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0



7. XNOR gate

$$y = A \odot B = AB + \bar{A}\bar{B}$$

A	B	$y = A \odot B$
0	0	1
0	1	0
1	0	0
1	1	1



XOR  
Just

$$AB + \bar{A}C = (A+B)(\bar{A}+C)$$

$$AB + \bar{A}C = B\bar{A} + \bar{A}C$$

Home work - Answers

$$1. (x+y)(x+yz')$$

$$= \bar{x}x + xy + xz + yz'$$

$$= x + x(y+z) + 0$$

$$= x + x$$

$$= \underline{\underline{x}}$$

$$2. xy + xyy'$$

$$= xy(1+y')$$

$$= \underline{\underline{xy}}$$

$$3) ABC + \bar{A}B + C(\bar{B} + \bar{A}C)$$

$$A) \bar{A}\bar{B} + \bar{A} + AB$$

$$= \bar{A} + \bar{B} + \bar{A} + AB$$

$$= \bar{A} + \bar{B} + AB$$

$$= \underline{\underline{\bar{A} + \bar{B} + AB}}$$

AND

Implement AND, OR, NOT, XOR operations in terms of NAND gates and NOR gates

OR  
Prove NAND and NOR gates are universal gates.

1) Using NAND gate

1) NOT gate

$$y = \bar{A}$$

for NAND gate

$$y = A\bar{B}$$

$$= \bar{A}A$$

$$= \underline{\underline{\bar{A}}}$$

Let  $[A=B]$



ii) AND gate

$$y = AB = \overline{\overline{AB}}$$







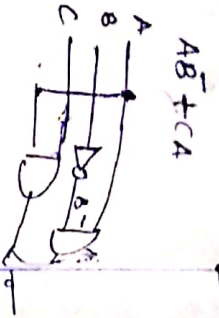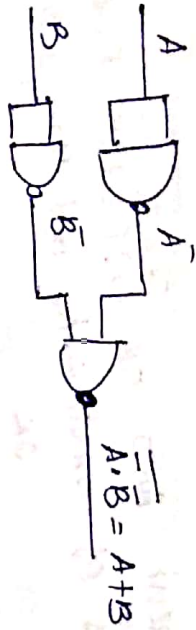iii) OR gate

$$y = A + B$$

$$= \overline{A \cdot B} = \overline{A} \cdot \overline{B} \text{ (DeMorgan's Law)}$$



iv)

XOR gate

$$y = A \oplus B$$


$$= \overline{A}B + A\overline{B}$$

$$= \overline{A}\overline{A} + \overline{A}B + A\overline{B} + B\overline{B}$$

$$= A(\overline{A} + B) + B(\overline{A} + \overline{B})$$

$$= A\overline{A}B + B\overline{A}B$$

$$= A\overline{A}B + B\overline{A}B$$

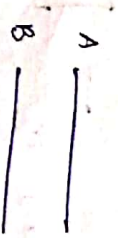

Using NOR

i) NOT gate

$$y = \overline{A + B}$$

$$(A = B)$$

$$= \overline{A + A}$$

$$= \overline{A}$$




ii)

AND gate

$$y = \overline{\overline{A}B} = \overline{\overline{A} + B}$$

(DeMorgan's)

$$y = A \cdot B$$

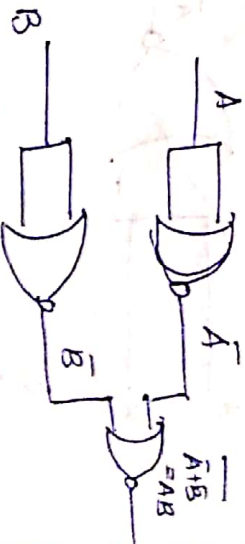

iii)

OR gate

$$y = A + B$$

$$= \overline{\overline{A + B}}$$



iv) XOR gate

$$Y = A \oplus B$$

$$= \bar{A}B + B\bar{A}$$

$$= \bar{A}\bar{1} + 1\bar{B} + \bar{0}A + 0\bar{B}$$


$$= \bar{A}(\bar{1} + B) + 0(\bar{A} + \bar{B})$$

$$= \bar{A}(\bar{1} + B) + B(\bar{A} + \bar{B})$$

$$= (\bar{A} + B)(\bar{A} + \bar{B})$$

$$= \overline{(\bar{A} + B)(\bar{A} + \bar{B})}$$
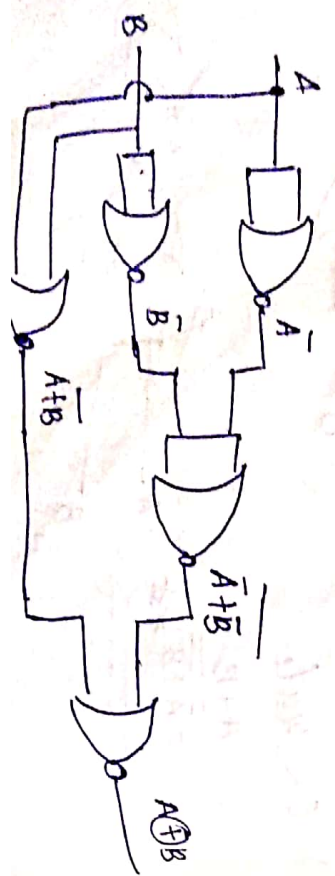
$$= \overline{(\bar{A} + B) + \bar{A} + \bar{B}}$$



SOP - sum of products form

Standard SOP =  $AB + B\bar{C} + \bar{A}C$

Canonical SOP =  $ABC + B\bar{C}A + \bar{A}BC$   
(sum of minterms)

POS - product of sums

Standard POS =  $(A + B)(B + C) \cdot A$

Canonical POS =  $(A + B + C)(A + \bar{B} + C)$   
(product of maxterms)

Each product term of canonical SOP is called Minterms  
Each sum term of canonical POS is called Maxterms

$\Rightarrow \Psi(A, B, C) = \bar{A}\bar{B} + BC \Rightarrow$  convert to canonical form.

$$\Psi(A, B, C) = \bar{A}\bar{B} + BC$$

$$= \bar{A}\bar{B}(C + \bar{C}) + BC(A + \bar{A})$$

$$= \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C} + ABC + \bar{A}B\bar{C}$$

$$= \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C} + ABC$$

$$= \overline{\bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C} + ABC} \text{ (Canonical SOP)}$$

$$\Rightarrow \Psi(A, B, C) = (A + B)(B + C)$$

$$= (A + \bar{B} + C)(A + B + \bar{C})$$

$$= \pi [0, 2, 3, 4] = \sum (1, 5, 6, 7)$$

(Apply distributive law)



$2^N$  - with  $2^N$  Max terms  
 $2^N - 1$  - with  $2^N - 1$  Min terms  
 Min terms:  $M_0 = A'B'C'$ ,  $M_1 = A'B'C$ ,  $M_2 = A'BC'$   
 Max terms:  $M_0 = A+B+C$ ,  $M_1 = A+B+C'$ ,  $M_2 = A+BC'$

$\Sigma$  Min terms (0-4)  
 $\Pi$  Max terms (0-4)  

A	B	C	$M_0 = A'B'C'$	$M_0 = A+B+C$
0	0	0	$M_1 = A'B'C$	$M_1 = A+B+C'$
0	0	1	$M_2 = A'BC'$	$M_2 = A+BC'$
0	1	0		
1	0	0	$M_3 = A'BC$	$M_3 = A'BC'$
1	0	1	$M_4 = A'BC'$	$M_4 = A'BC$
1	1	0	$M_5 = A'BC$	$M_5 = A'BC'$
1	1	1	$M_6 = A'BC'$	$M_6 = A'BC$
			$M_7 = ABC$	$M_7 = A+BC'$

$\Rightarrow f(A,B,C) = ABC + \bar{A}B\bar{C} + \bar{A}BC$   
 $= m_7 + m_2 + m_3$   
 $= \Sigma m(2,3,7)$

$\Rightarrow M = xy + x'z$

Express the function in sum of minterms and product of max terms.

$M = xy + x'z$   
 $= xy(x+z) + x'z(x+y)$   
 $= xyz + xyz' + x'xy + x'zy$

$000-x'$   
 $01-x'z$   
 $10-xy$   
 $11-x'y$


$\Rightarrow 0-1$   
 $= xyx + xyx' + x'yz + x'yz'$   
 $= m_7 + m_6 + m_3 + m_1$

$M = \Pi M(0,2,4,5)$


$\Rightarrow f(A,B,C,D) = B'B + AB + BD$   
 $\Rightarrow f = A+B'C$

# K-Map (Karnaugh Map)

1. 2 variable k-map

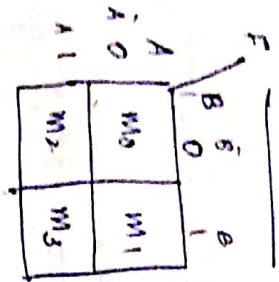

2. 3 variable k-map

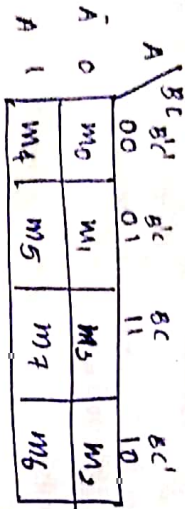


1. Simplify using k maps

$$F(x,y) = \sum(1,2,3)$$

$$F = m_1 + m_2 + m_3$$

$$= \bar{x}y + x\bar{y} + xy$$


k-map

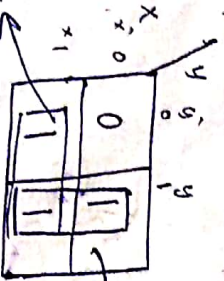

$$m_2 + m_3 = x\bar{y} + xy = (x+y)x = x$$

$$m_1 + m_3 = \bar{x}y + xy = (\bar{x}+x)y = y$$


$$F = x + y$$

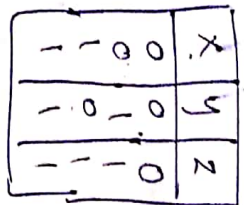

$$F = \sum(1,2,3)$$


$$\pi(0)$$

2.  $F(x,y,z) = \sum(2,3,4,5)$

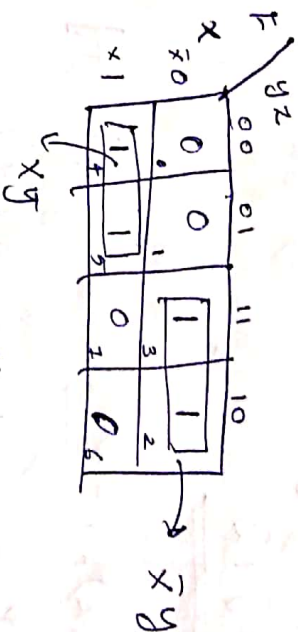

$$F = \bar{x}y + xy$$


3.  $F = \sum(3,4,6,7)$

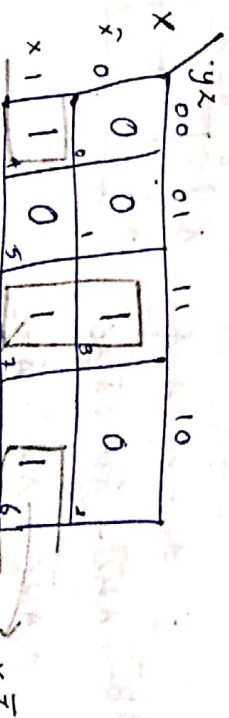

$$F = x\bar{z} + yz$$



4)  $F(x,y,z) = \sum (0, 2, 4, 5, 6)$

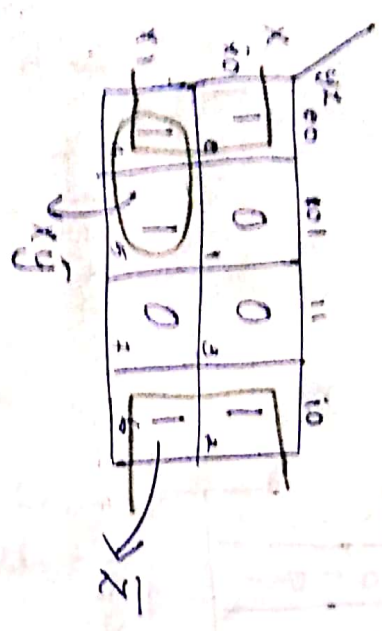

$F = x\bar{y} + \bar{z}$

5)  $F(x,y,z) = 1 \Rightarrow$

$F = \sum (0, 1, 2, 3, 4, 5, 6, 7)$



6)  $F = A\bar{C} + \bar{A}B + A\bar{B}C + BC$

$= A\bar{C}(B+\bar{B}) + \bar{A}B(C+\bar{C})$

$+ A\bar{B}C + BC(A+\bar{A})$



$= A\bar{B}C + A\bar{B}\bar{C} + \bar{A}BC + \bar{A}B\bar{C}$

$+ A\bar{B}C + A\bar{B}\bar{C} + \bar{A}BC$

$= A\bar{B}\bar{C} + A\bar{B}C + \bar{A}BC + \bar{A}B\bar{C} + A\bar{B}C + A\bar{B}\bar{C} + \bar{A}BC + \bar{A}B\bar{C}$




Apply Karnaugh map

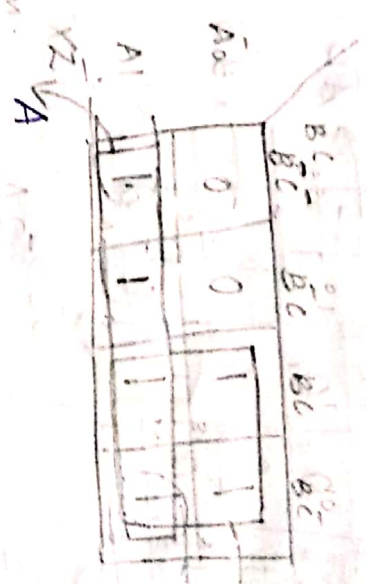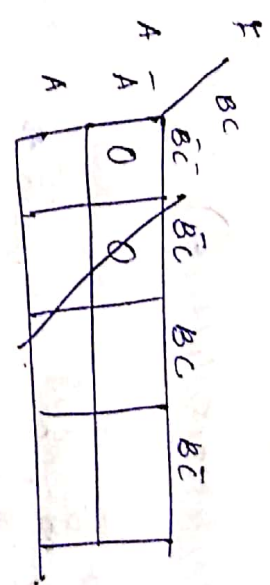

$F = A + B$

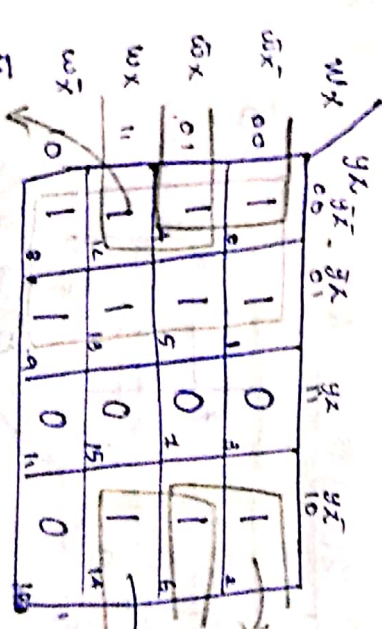7)  $F(w,x,y,z) = \sum (0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$




$F = \bar{w}\bar{z} + x\bar{z} + \bar{w}\bar{z} + x\bar{z} + y\bar{z}$



8)  $f = f(A, B, C, D)$


$= \sum (0, 2, 3, 4, 6, 8, 11, 12, 14)$

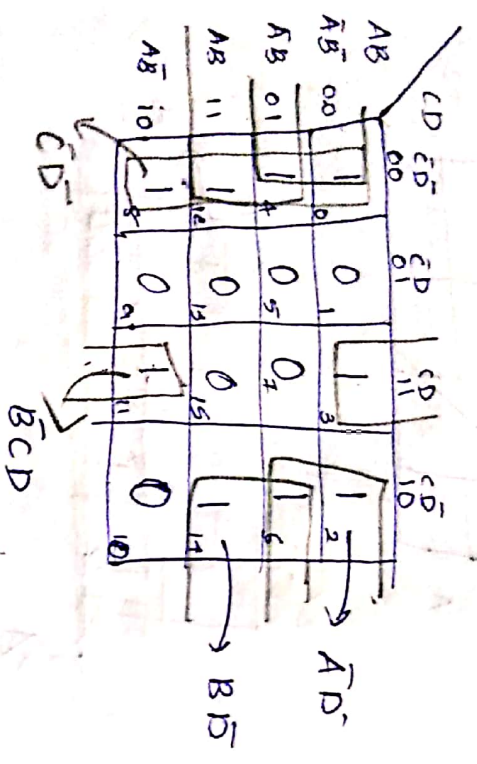

$f = A\bar{B} + C\bar{B} + B\bar{C} + B\bar{D}$

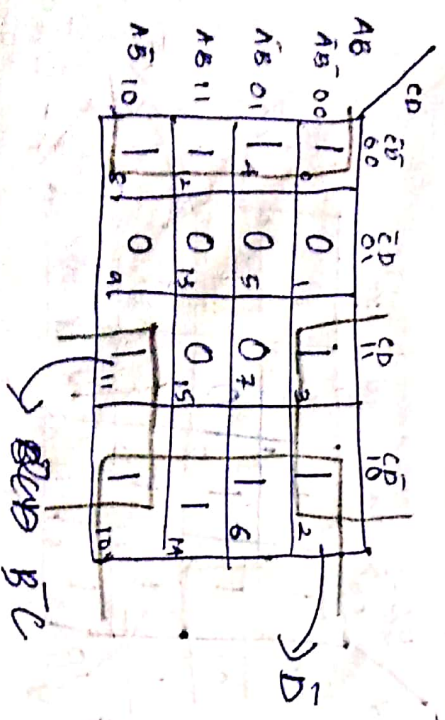9) Simplify

$f(A, B, C, D) = \pi (1, 5, 7, 9, 13, 15)$  to SOP form  
 $= \sum (0, 2, 3, 4, 6, 8, 10, 11, 12, 14)$



~~$f = \bar{B}\bar{C}D$~~

$f = \bar{B}\bar{C} + D$

function 'f' from k-map

1. 'f' in SOP form

solve for case, product term

2. 'f' in POS form

solve for zeros, sum term

F from k map

1. F in SOP form

solve for 0's, product term

2. F in POS form


solve for 1's, sum term

1. Implement the following functions  $f$  and its complement  $\bar{f}$  using NAND gate and NOR gate. Find SOP and POS forms of  $f$  and  $\bar{f}$

$f(x,y,z) = \sum(0,6)$


NAND  $\rightarrow$  SOP  
NOR  $\rightarrow$  POS

1)  $f$  in SOP form

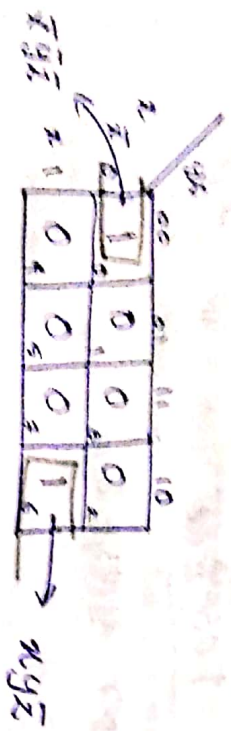

$f = \bar{x}\bar{y}\bar{z} + x\bar{y}\bar{z}$

2)  $\bar{f}$  in POS form

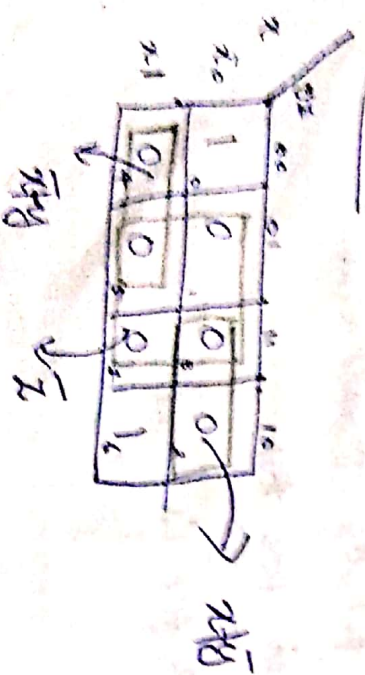

$\bar{f} = (\bar{x} + y) \cdot \bar{z} (x + \bar{y})$


3)  $\bar{f}$  in SOP form

$$F = \bar{x}\bar{y}\bar{z} + x\bar{y}\bar{z}$$

$$= \bar{x} + y + z + \bar{x} + \bar{y} + z$$


$$= x\bar{y} + z + \bar{x}\bar{y}$$

3)  $\bar{f}$  in POS form

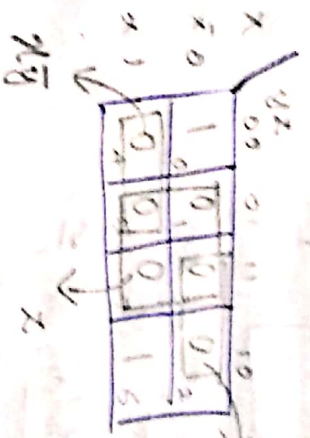

$\bar{f} = x\bar{y} + z + \bar{x}\bar{y}$


4)  $\bar{f}$  in POS form

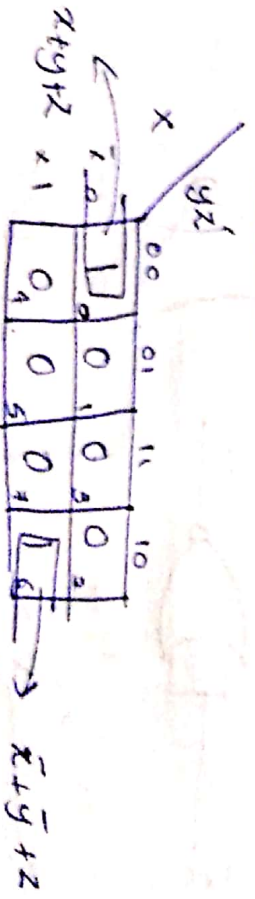


$f = (x + y + z) \cdot (\bar{x} + \bar{y} + z)$



## NAND implementation of F

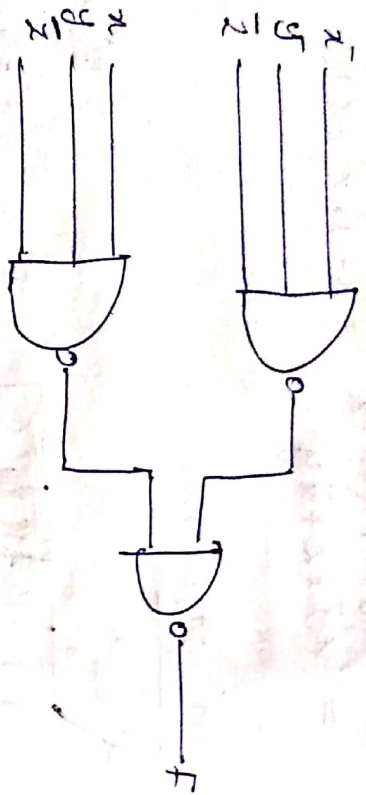

## NOR implementation of F

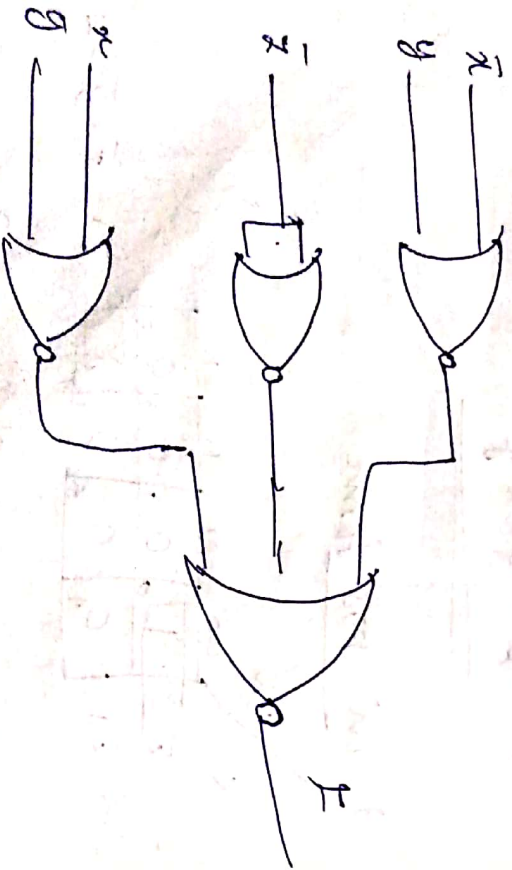

⇒ Simply the following function

### Don't care conditions

There are some applications where functions are not specified for a certain combinations of variables. Since these unallowed states will never require to occur in our application they can be treated as don't care term w.r.t their effect on the output. i.e. for these don't care term either a '1' or a '0' may be assigned to the output. It really doesn't matter since they will never occur. To distinguish don't care conditions from '1' and '0's a symbol 'x' is used. to represent.

$$1. f(w, x, y, z) = \sum (1, 3, 7, 11, 15)$$

$$d(x, y, z) = \sum (0, 2)$$

yz

00	01	11	10
00	1	1	x
01	0	0	0
11	0	1	1
10	0	0	0
00	0	0	0
01	0	0	0
11	0	0	0
10	0	0	0

wx

$$f = \bar{w}\bar{x} + yz$$




2. simplify the following function  $f(A, B, C, D)$   
 $= \sum(6, 7, 8, 9)$

assuming that the condition having both  $A=0$  and  $B=0$  can never occur. Also realize the circuit using NAND gate.

$A=0, B=0 \Rightarrow$  never occur  


A	B	C	D	
0	0	0	0	$\rightarrow m_0$
0	0	0	1	$\rightarrow m_1$
0	0	1	0	$\rightarrow m_2$
0	0	1	1	$\rightarrow m_3$

 don't care

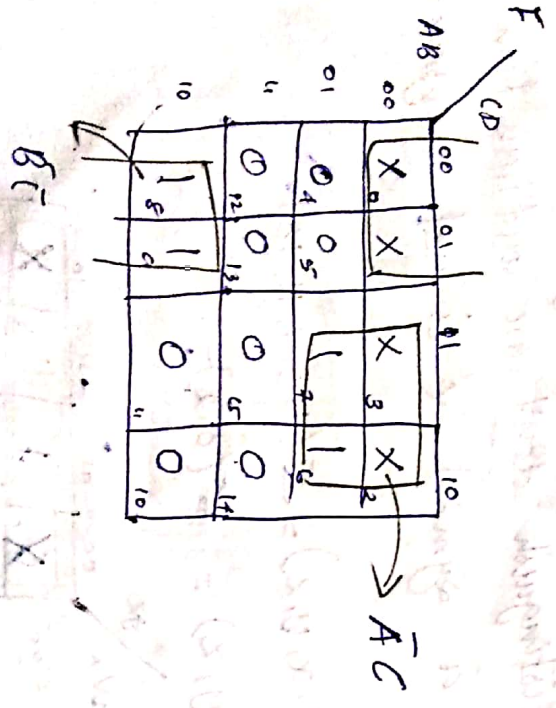

$F = B\bar{C} + \bar{A}C$

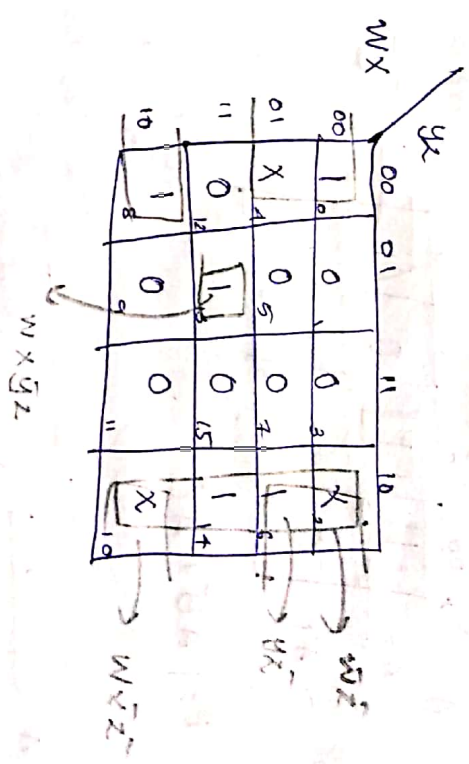3.  $f = \sum(0, 6, 8, 13, 14)$   
 $d = \sum(2, 4, 10)$




4. Design a circuit with 3 input and one output

Then o/p is 1, when binary value of i/p is  $< 3$   
 The o/p is 0, otherwise.


i/p      o/p

A	B	C	f
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

$F = \Sigma (0, 1, 2)$

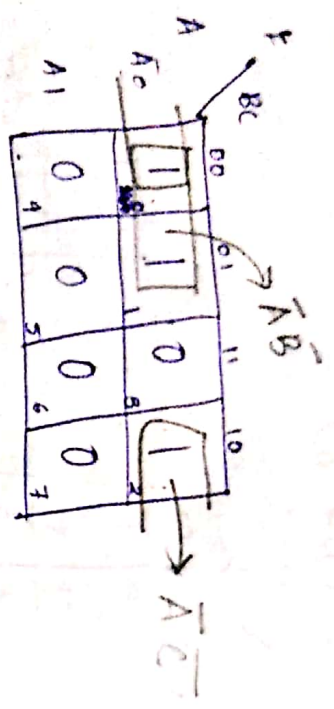

$F = \bar{A}\bar{B} + \bar{A}\bar{C}$

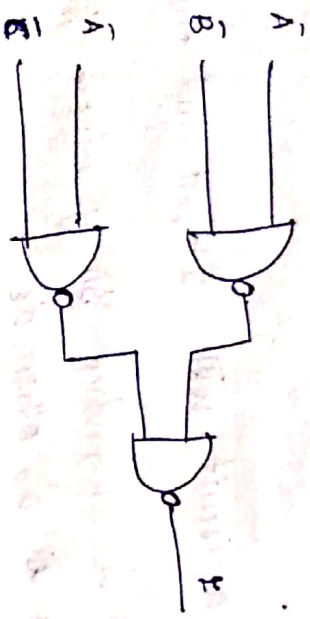

MP  
 Quine - McCluskey Method (Tabulation Method)  
 => simplify the function  $f = \Sigma (0, 1, 6, 7, 8, 9, 13, 14, 15)$   
 using tabulation method.

$f = \Sigma 0, 1, 6, 7, 8, 9, 13, 14, 15$

0 - 0000	Index 0 - 0
1 - 0001	1 - 1, 8
6 - 0110	2 - 6, 9
7 - 0111	3 - 7, 14, 13
8 - 1000	4 - 15
9 - 1001	
13 - 1101	
14 - 1110	
15 - 1111	

1001 + 1  
 0101 + 1  
 0111 + 1  
 1100 + 1  
 1101 + 1  
 1110

Index	Minterm	Binary designation ABCD	
Index 0	0	0000 ✓	(0,1) 000 - (0,8) -000 ✓ 1110 f 0118 a 00119 0002
Index 1	8	0001 ✓	(1,9) -001 ✓
Index 2	6, 9	0110 ✓ 1001 ✓	(6,7) 011 - (6,14) -110 ✓ (9,13) 1001 (6,14) 011 - (6,14) 110 - (6,14) 111 -
Index 3	7, 13, 14	0111 ✓ 1101 ✓ 1110 ✓	(3,15) -111 (3,15) 011 -1 (14,15) -111 -
Index 4	15	1111 ✓	(14,15) 111 -



Prime implicants

- P 1-01 A $\bar{C}$ D
- Q 11-1 ABD
- R -00-  $\bar{B}\bar{C}$
- S -11- BC

Prime Implicants Chart

	0	1	6	7	8	9	13	14	15
(9,13) A $\bar{C}$ D						X	X		
(3,15) ABD							X		X
(9,11,13) $\bar{B}\bar{C}$	X	X			X	X			
(1,3,14,15) BC		X	X	X				X	X

$F = \bar{B}\bar{C} + BC + A\bar{C}D$

OR

$F = \bar{B}\bar{C} + BC + ABD$

BC = 1 0  
 0 1  
 0 + 0  
 0 1  
 0 1  
 0 1

2) simplify using tabulation method

$F(w,x,y,z) = \sum(1,4,5,7,9,10,11,15)$

Index	Index	Index
1-0001	1-1,4,8	1
4-0100	2-6,9,10	2
6-0110	3-7,11	3
7-0111	4-15	4
8-1000		
9-1001		
10-1010		
11-1011		
15-1111		

Minterms

Index	Minterms
Index 1	(1,9) (8) F (4,6) (2) Q (2,10) (2) R (2,9) (1) S
Index 2	(6,7) (1) R (9,11) (2) S (10,11) (1) T
Index 3	(3,15) (8) J (11,15) (4) T
Index 4	15

Always take lower digit  
 Always take lower digit  
 Always take lower digit



Prime Implicants

0111  
1111  
1000  
0100  
0001

P - (1,9)(8)	wxyz	-001	→	$\bar{x}\bar{y}z$
Q - (4,6)(2)		01-0	→	$w\bar{x}\bar{z}$
R - (6,7)(1)		011-	→	$w\bar{x}y$
S - (3,15)(5)		-111	→	$x\bar{y}z$
T - (11,15)(4)		1-11	→	$wyz$

Essential Prime Implicants

$\bar{x}\bar{y}z$   
 $w\bar{x}\bar{z}$   
 $x\bar{y}z$   
 $w\bar{x}$

$f = \bar{x}\bar{y}z + w\bar{x}\bar{z} + x\bar{y}z + w\bar{x}$

3)  $F = \Sigma(6,7,8,9) + d(10,11,12,13,14,15)$

6-0110	Index
7-1110	1-8,
8-1000	2-6,9,10,12,
9-1001	3-7,11,13,14,
10-1010	4-15
11-1011	
12-1100	
13-1101	
14-1110	
15-1111	

U (8,9,10,11)(6,11)	10--	→	$w\bar{x}$
* (1,9) $\bar{x}\bar{y}z$	1	X	
* (4,6) $w\bar{x}\bar{z}$	4	X	
(6,7) $w\bar{x}y$	6	X	
* (7,15) $x\bar{y}z$	7	X	
(11,15) $wyz$	8	X	
* (8,9,10,11) $w\bar{x}$	9	X	
	10	X	
	11	X	
	15	X	

Students	Minterms		
Student 1	8 ✓ 9 ✓ 10 ✓ 12 ✓	(8,9) (11) ✓ (8,10) (8,2) ✓ (8,12) (4) ✓	(8,10,9,11) (2,11) ✓ (8,9,10,11) (1,5,2) ✓ (8,9,12,13) (1,1,4) ✓ (8,12,10,14) (4,12) ✓
Student 2	6 ✓ 9 ✓ 10 ✓ 12 ✓	(6,7) (12) ✓ (6,14) (8) ✓ (9,11) (2) ✓ (9,13) (4) ✓ (10,11) (1) ✓ (10,13) (2) ✓ (10,15) (8) ✓ (11,15) (4) ✓	(10,14,14,15) (8,14) ✓ (6,14,7,15) (8,1) ✓ (9,13,11,15) (4,12) ✓ (9,11,13,15) (2,1,4) ✓ (2,11,3,14,15) (1,2) ✓
Student 3	7 ✓ 11 ✓ 13 ✓ 14 ✓	(7,15) (8) ✓ (11,15) (4) ✓ (13,15) (2) ✓ (14,15) (4) ✓	
Student 4	15 ✓		010 011 010 100 100

Prime implicants

(6,7,14,15) (8,11)  $wxyz$   
 ---  
 →  $xy$

(8,9,10,11,12,13,14,15) (1,2,4)  $wxyz$   
 ---  
 →  $w$

(6,14,7,15) (8,11)  $wxyz$   
 ---  
 →  $w$

(8,9,10,11,12,13,14,15)  $wxyz$   
 ---  
 →  $w$

(8,9,10,11,12,13,14,15) (1,2,4)  
 (8,9,10,11,12,13,14,15)

Essential Prime Implicants


$F = w + xy$

1. Design a combinational circuit with 3 inputs and one output. The output is '1' when majority of inputs are high, otherwise the output is '0'.

input	output
A B C	F
0 0 0	0
0 0 1	0
0 1 0	0
0 1 1	1
1 0 0	0
1 0 1	1
1 1 0	1
1 1 1	1




$$F = \Sigma(3, 5, 6, 7)$$

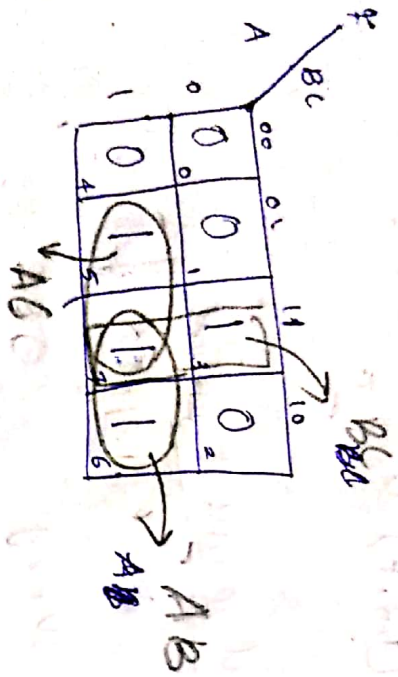


$$F = A + BC$$

$$F = A\bar{B}\bar{C} + A\bar{B}C + AB\bar{C} + ABC$$

$$F = AC + AB + BC$$

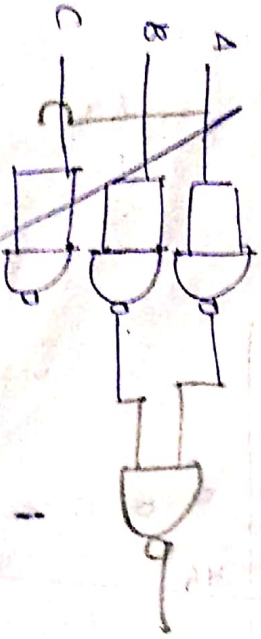


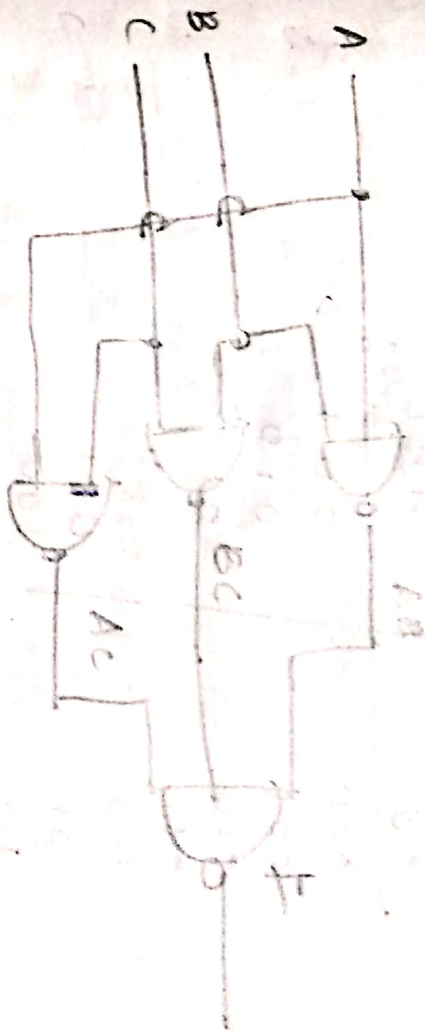2. Design a circuit with 3 inputs  $x, y, z$  & 3 outputs  $A, B, C$ . when the binary input is 0, 1, 2 or 3, the binary output is '1' greater than the input. when the binary input is 4, 5, 6, or 7 the binary output is '1' less than the input.







i/p	xyz	A B C
000	001	
001	010	
010	011	
011	100	
100	011	
101	100	
110	101	
111	110	

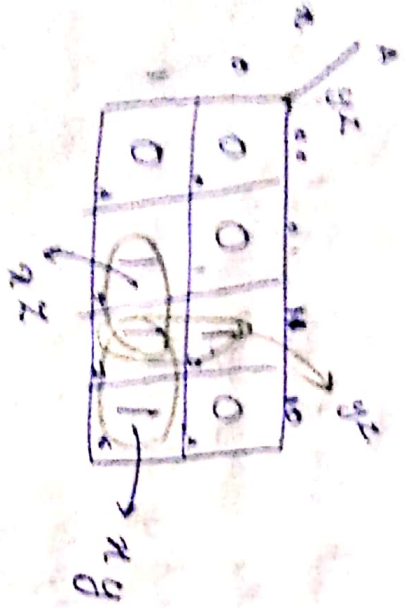

A = yz + xz + xy

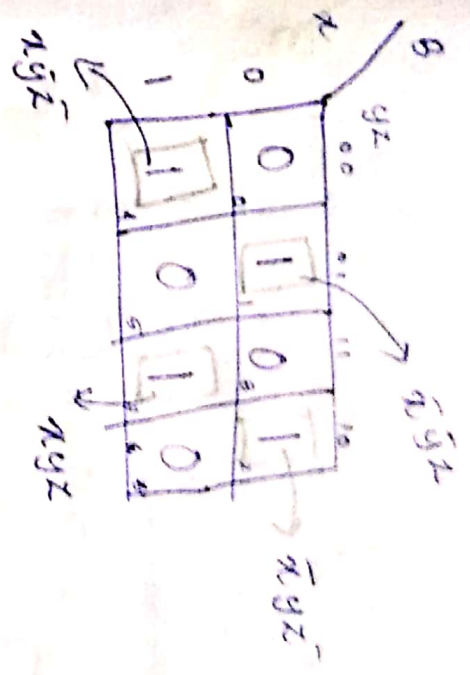

B = x y z̄ + x̄ y z + x̄ y z̄

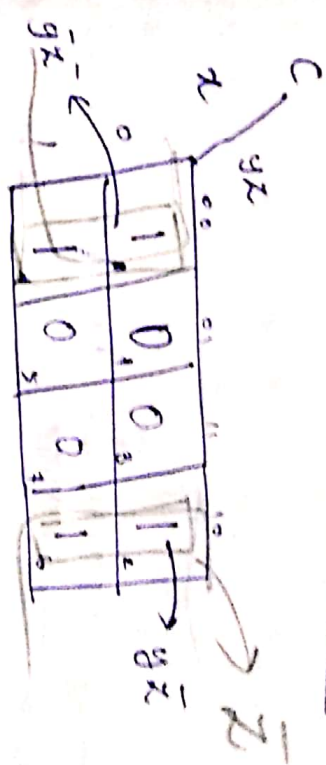

C = y z̄ + y z + x z̄  
= z̄

